

# **Chapter 4**

# **CPU DESIGN**

Assistant Professor  
Er. Shiva Ram Dam

# Contents:

1. Introduction to CPU
2. Specifying a CPU
3. Design and Implementation of a Very Simple and Relatively Simple CPU
4. Instruction Execution, Fetch, Decode , Data path
5. ALU Design
6. Designing Hardwired Control Unit
7. Design Verification


# 4.1 Introduction to CPU

- ALU + Registers + Control Unit
- Performs sequences of microoperations needed to perform fetch, decode and execute cycles of every instructions in CPU instruction set.
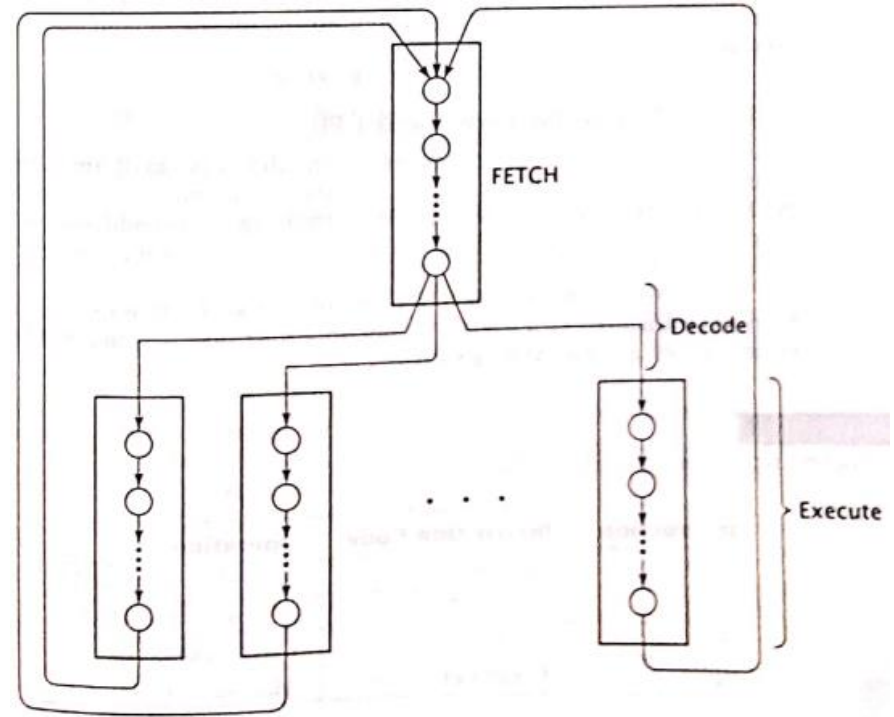
## 4.2 Specifying a CPU

- The first step in designing CPU is to **determine its applications**. The key is to match the capabilities of the CPU to the tasks it will perform.
- Second step is to **design a Instruction Set Architecture (ISA)** which can handle the given tasks.
- Third step is to **design State diagram for CPU**. Here the different microoperation are shown which are performed during each stat and the conditions that cause CPU to go from one state to another. CPU is a complex Finite State Machine.
- Then, specifying the steps the CPU must perform in order to fetch, decode and execute every instructions in its instruction set.

- In general, a CPU performs following sequence of operations.
  1. **Fetch Cycle:** Fetching an instruction from memory, then go to decode cycle.
  2. **Decode Cycle:** Decoding an instruction- that is, determine which instruction has been fetched.
  3. **Execute cycle:** Executing the instruction . Then go to the fetch cycle and fetch the next instruction.



Generic CPU state diagram

## 4.3 Design and Implementation of a Very Simple and Relatively Simple CPU

- To illustrate the CPU design process,
- lets us consider:
  - A small and somewhat impractical CPU.
  - It can access 64 bytes of memory, each byte being 8 bits wide.
  - The CPU does this by outputting a 6-bit address on its output pins A[5..0], and reading in the 8-bit value from memory on its inputs D[7...0].
  - The CPU has: one programmable register, 8-bit accumulator (AC).
  - It has only four instructions in its instruction set.

Instruction	Instruction Code	Operation
ADD	00AAAAAA	$AC \leftarrow AC + M[AAAAAA]$
AND	01AAAAAA	$AC \leftarrow AC \wedge M[AAAAAA]$
JMP	10AAAAAA	GOTO AAAAAA
INC	11XXXXXX	$AC \leftarrow AC + 1$

Instruction set for the Very Simple CPU

# Design and Implementation of a Very Simple and Relatively Simple CPU

- In addition to AC, the CPU contains the following registers:
  1. **Address Register (AR):**
    - 6-bit
    - Supplies an address to memory via A[5..0].
  2. **Program Counter(PC):**
    - 6-bit
    - Contains the address of the next instruction to be executed.
  3. **Data Register(DR):**
    - 8-bit
    - Receives instructions and data from memory via D[7...0]
  4. **Instruction Register(IR):**
    - 2-bit
    - Stores the opcode portion of the instruction code fetched from memory.

## 4.4 Instruction Execution, Fetch, Decode and Datapath

- Fetching instructions from memory
- Decoding instructions
- Executing instructions
- Constructing Datapath



# 1. Fetching instructions from Memory.

- The address of instruction to be fetched is stored in the PC. Since, address register (AR) supplies an address to memory through A [5.....0] pins
- Firstly, copy the content of PC to AR.


**Fetch 1:**      $AR \leftarrow PC$

- The CPU reads the instructions from the memory and store in Data Register (DR).

**Fetch 2:**      $DR \leftarrow M$   
                   $PC \leftarrow PC + 1$

- Finally, two higher order bits of DR are copied into Instruction Register (IR); these two bits indicate which instruction is to be executed, and the CPU copies the lower order 6-bit of DR into AR.

 
**Fetch 3:**      $IR \leftarrow DR [7,6]$   
                   $AR \leftarrow DR [5....0]$



Fetch cycle for the Very Simple CPU
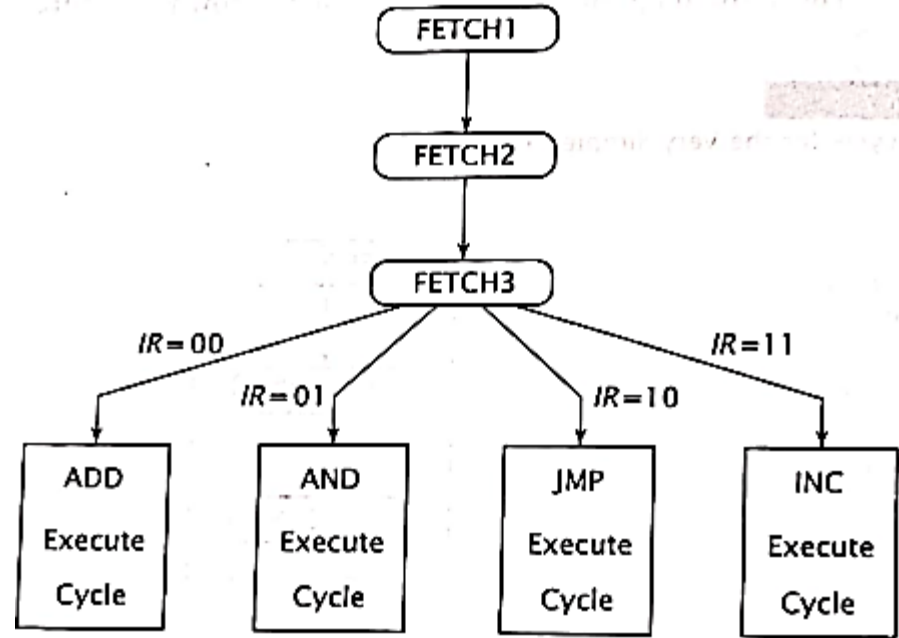
## 2. Decoding instructions

- After CPU has fetched an instruction from memory, it must determine which instruction it has fetched so that it may invoke the correct **execute routine**.
- For this CPU, there are four instructions and thus, four executer routines.
- The value in IR (00,01,10 or 11) determines which execute routine is invoked.



Fetch and decode cycles for the Very Simple CPU

### 3. Executing instructions

- To complete the state diagram for this CPU, we must develop the state diagram for each execute routine.
- Now we design the portion of the state diagram for each routine and the overall design for the CPU.
- The state diagrams for the individual execute routines are fairly simple, so they are only included in the diagram of the finite state machine for the entire CPU.

## a) ADD instruction

- To perform ADD instruction, CPU must :
- First, fetch one operand from memory.
- Then add this operand to current contents in AC and store result back in the AC.

**ADD1:  $DR \leftarrow M$**

**ADD2:  $AC \leftarrow AC + DR$**

## b) AND instruction

- Virtually similar to ADD instruction.
- First, fetch an operand from memory.
- Logically AND the two values and store it in AC.

**AND1:  $DR \leftarrow M$**

**AND2:  $AC \leftarrow AC \wedge DR$**

## c) JMP instruction

- The address to which the CPU must jump is copied into the PC.
- Then CPU fetches the next instruction.

**JMP1:  $PC \leftarrow DR[5..0]$**

## d) INC instruction

- CPU simply adds 1 to contents of AC and goes to fetch routine.

**INC1:  $AC \leftarrow AC + 1$**


# Establishing required Data paths

- The state diagram and register transfers specify what must be done in order to realize this CPU.
- Now we must design the CPU so that it actually does these things.
- First, we look at what data transfers can take place and design the internal data paths of the CPU so this can be done.
- The operations associated with each state for this CPU are:

```
FETCH1:  $AR \leftarrow PC$   
FETCH2:  $DR \leftarrow M, PC \leftarrow PC + 1$   
FETCH3:  $IR \leftarrow DR[7..6], AR \leftarrow DR[5..0]$   
ADD1:  $DR \leftarrow M$   
ADD2:  $AC \leftarrow AC + DR$   
AND1:  $DR \leftarrow M$   
AND2:  $AC \leftarrow AC \wedge DR$   
JMP1:  $PC \leftarrow DR[5..0]$   
INC1:  $AC \leftarrow AC + 1$ 
```



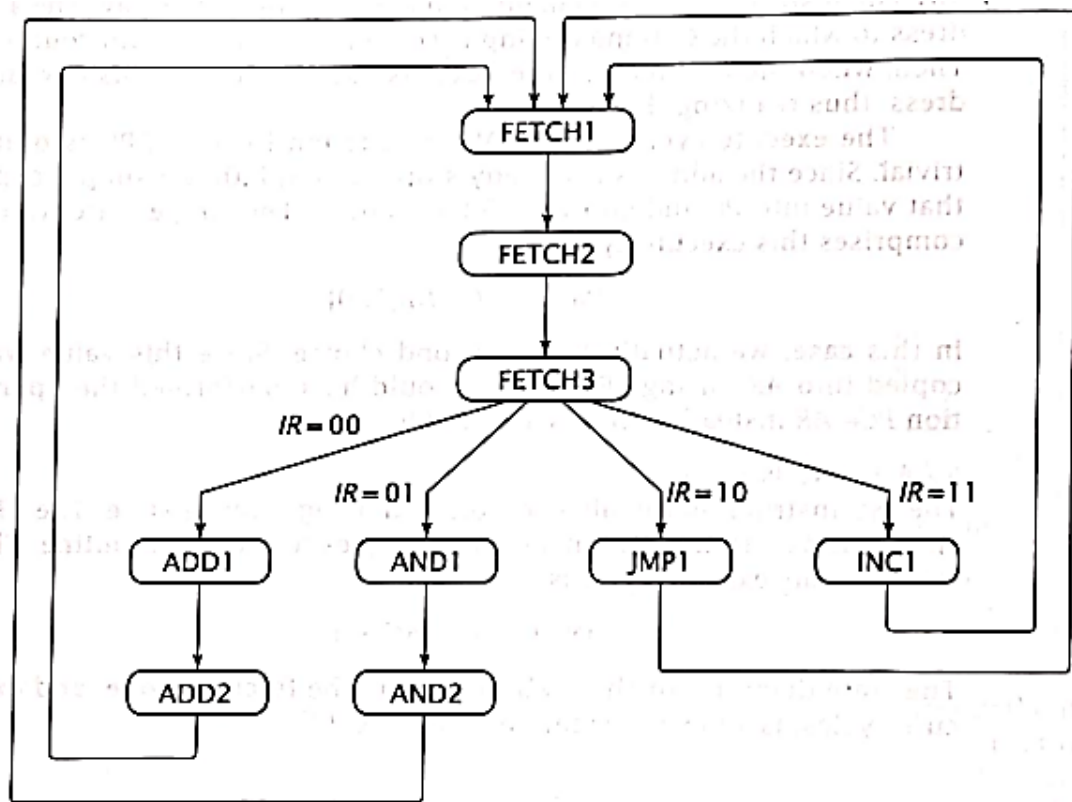FETCH1:  $AR \leftarrow PC$   
 FETCH2:  $DR \leftarrow M, PC \leftarrow PC + 1$   
 FETCH3:  $IR \leftarrow DR[7..6], AR \leftarrow DR[5..0]$   
 ADD1:  $DR \leftarrow M$   
 ADD2:  $AC \leftarrow AC + DR$   
 AND1:  $DR \leftarrow M$   
 AND2:  $AC \leftarrow AC \wedge DR$   
 JMP1:  $PC \leftarrow DR[5..0]$   
 INC1:  $AC \leftarrow AC + 1$



Complete state diagram for the Very Simple CPU

- To design the data paths, we can take one of two approaches.
  - Create **direct paths** between each pair of components that transfer data.
  - Create a **bus** within the CPU and route data between components via the bus.

- Now we regroup the operations, without regard for the cycles in which they occur, by the register whose contents they modify. This results in the following:

FETCH1:  $AR \leftarrow PC$   
FETCH2:  $DR \leftarrow M, PC \leftarrow PC + 1$   
FETCH3:  $IR \leftarrow DR[7..6], AR \leftarrow DR[5..0]$   
ADD1:  $DR \leftarrow M$   
ADD2:  $AC \leftarrow AC + DR$   
AND1:  $DR \leftarrow M$   
AND2:  $AC \leftarrow AC \wedge DR$   
JMP1:  $PC \leftarrow DR[5..0]$   
INC1:  $AC \leftarrow AC + 1$



AR:  $AR \leftarrow PC; AR \leftarrow DR[5..0]$   
PC:  $PC \leftarrow PC + 1; PC \leftarrow DR[5..0]$   
DR:  $DR \leftarrow M$   
IR:  $IR \leftarrow DR[7..6]$   
AC:  $AC \leftarrow AC + DR; AC \leftarrow AC \wedge DR; AC \leftarrow AC + 1$

AR:  $AR \leftarrow PC$ ;  $AR \leftarrow DR[5..0]$


PC:  $PC \leftarrow PC + 1$ ;  $PC \leftarrow DR[5..0]$

DR:  $DR \leftarrow M$

IR:  $IR \leftarrow DR[7..6]$

AC:  $AC \leftarrow AC + DR$ ;  $AC \leftarrow AC \wedge DR$ ;  $AC \leftarrow AC + 1$

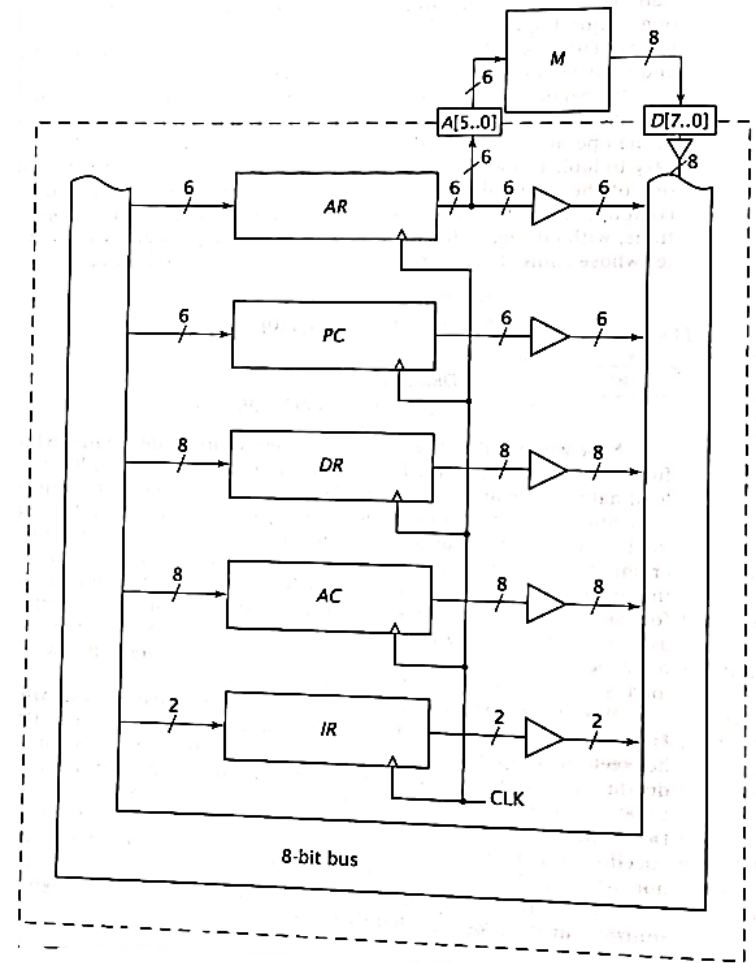
- AR, DR and IR always load data from some other component.
- We connect every component to the system bus, as shown in figure.
- We include tri-state buffers to restrict data being placed all the times by everyone.
- Also, the output of AR are connected to pins A[5..0], as required in the CPU specification.



Preliminary register section for the Very Simple CPU

AR:  $AR \leftarrow PC; AR \leftarrow DR[5..0]$   
 PC:  $PC \leftarrow PC + 1; PC \leftarrow DR[5..0]$   
 DR:  $DR \leftarrow M$   
 IR:  $IR \leftarrow DR[7..6]$   
 AC:  $AC \leftarrow AC + DR; AC \leftarrow AC \wedge DR; AC \leftarrow AC + 1$

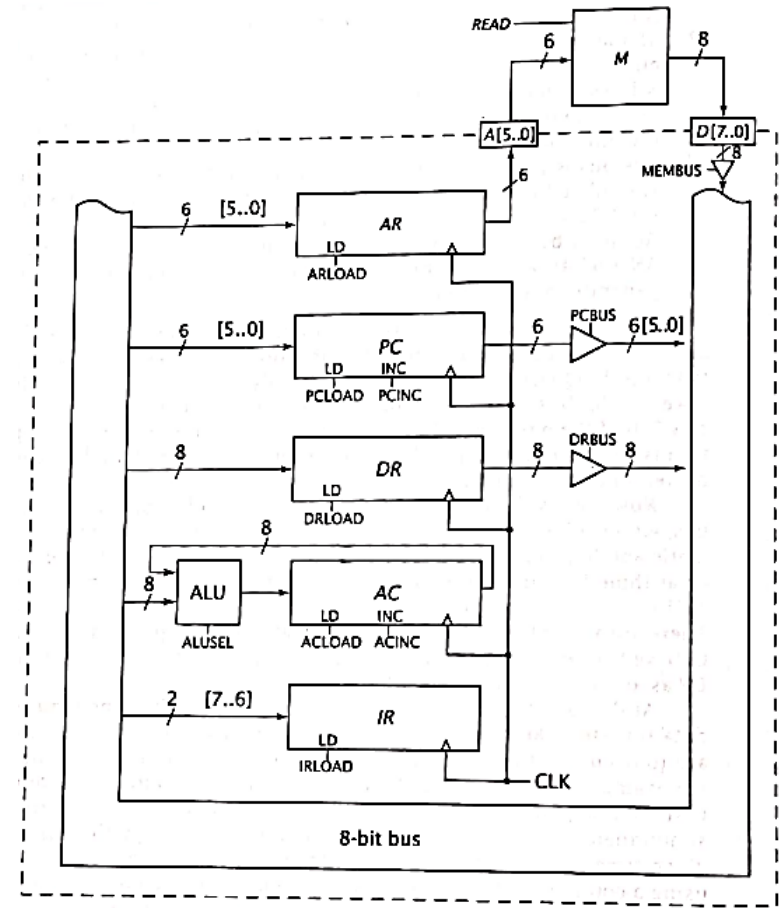
- AC can load in one of two values, either  $AC+DR$  or  $AC \wedge DR$ .
- The CPU must incorporate some arithmetic and logic circuitry to generate these values.
  - When  $ALUSEL = 0$ , the output of ALU is arithmetic sum of its input
  - When  $ALUSEL = 1$ , the output of ALU is logical AND of its input.



Final register section for the Very Simple CPU
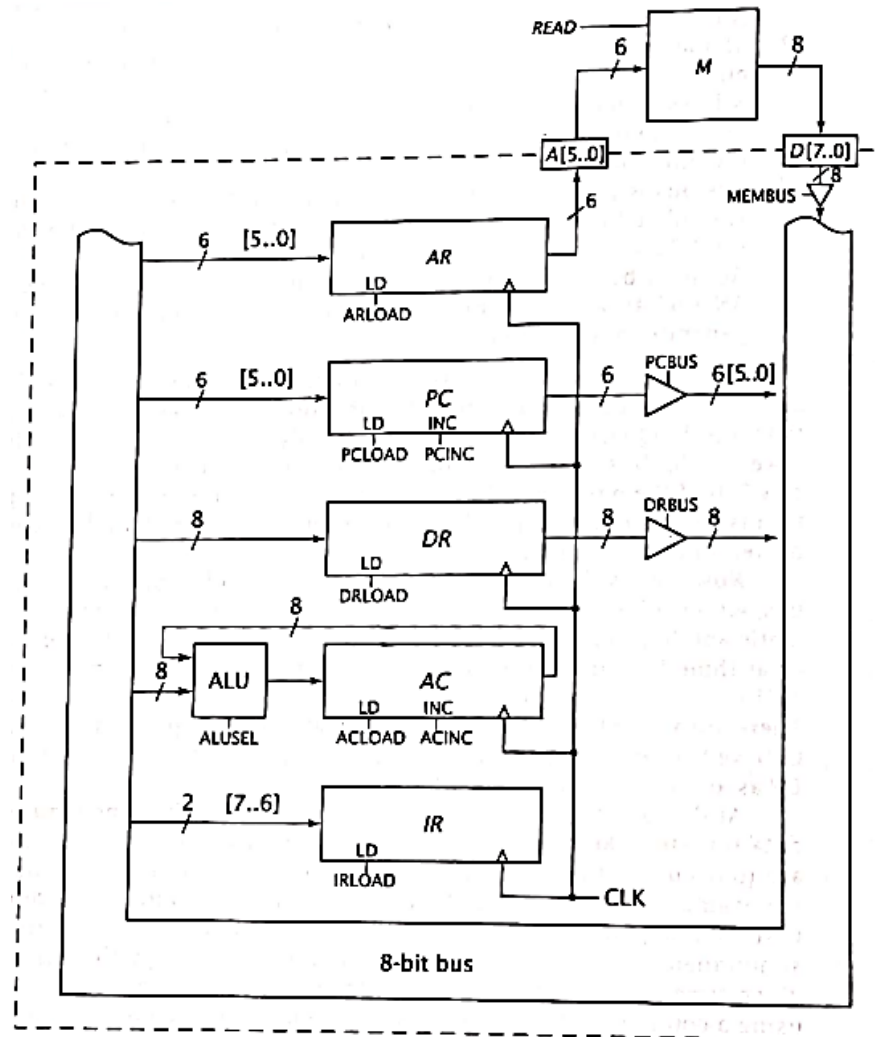
## 4.5 ALU Design

- The circuit diagram for the relatively simple CPU is shown in figure below:



# ALU for relatively simple CPU

- The ALU for this CPU performs only two functions:
  - Adds its two inputs or
  - logically ANDs its two inputs.
- The simplest way to design this ALU is to create separate hardware to perform each function and then use a multiplexer to output one of the two results.
  - The addition is implemented using a standard 8-bit parallel adder.
  - The logical AND operation is implemented using eight bits 2-input AND gates.
  - The outputs of the parallel adder and the AND gates are input to an 8-bit 2 to 1 multiplexer.
  - The control unit of the MUX is called S (for select).



 


Figure: ALU Design

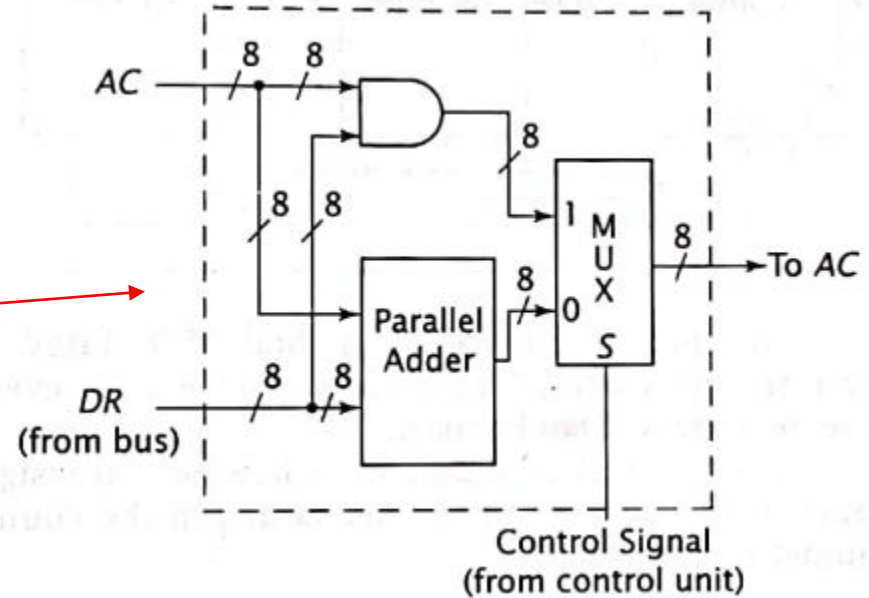

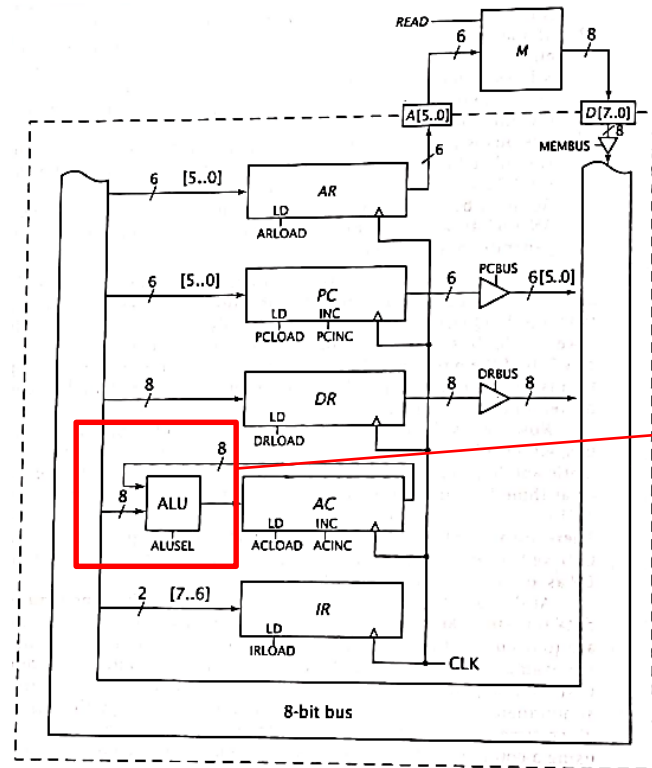

## 4.6 Designing Hardwired Control Unit


- After designing the CPU for every operation necessary to fetch, decode and execute the entire instruction set, the next step is **to design the circuit to generate control signals to cause operation to occur in proper sequence**. This is control unit.
- There are two methods:
  - Hardwired control
  - Microprogrammed control
- Hardwired control:
  - It uses sequential and combinational logic to generate control signals.
- Microprogrammed control:
  - It uses a lookup memory to output the control signals.

## 4.6 Designing Hardwired Control Unit (Contd.)

- Here, we focus on **hardwired control**.
- The simple control unit has three components:
  - a) **Counter:** it contain current state.
  - b) **Decoder:** It takes current state and generates individual signals for each state.
  - c) **Combinational Logic:** It takes the individual state signals and generate the control signals for each component as well as the signals to control the counter.
- These signals cause control unit to traverse the states in proper order.
 
# Generic Hardwired Control Unit

- The CPU that we have designed has 9 total states. So, a 4-bit counter and 4-to-16 decoder are needed. Here, seven of the outputs of the decode will not be used.
- **Input:** in input, states are provided.
- **CLK:** a clock signal
- **CLR:** CLR input is used to reach the state needed.
- **INC:** use INC input of counter to traverse the states.
- **LD:** use LD input to reach the proper execute routine.



# Mapping Logic

- To make the function simple as possible:
- Consider the possible mapping 10 IR [1...0] i.e. if IR=00, the input to counter is 1000. For IR=01, the input is 1001 and so on.
- So, the counter values will be:

IR	Counter value	state
00	10 <u>00</u> (8)	ADD1
01	10 <u>01</u> (9)	AND1
10	10 <u>10</u> (10)	JMP1
11	10 <u>11</u> (11)	INC1


Counter values for  
the proposed mapping function

- Here, the problem arises. Since state ADD1 has a counter value of 8 and state AND1 has a counter value of 9. There is no counter value that has to be assigned to ADD2. (not best solution)


- Now if we mapping function as: 1IR [1... 0]0, which results in counter values of:

IR	Counter	Value	state
00	1 <u>00</u> 0 (8)	8	ADD1
01	1 <u>01</u> 0 (10)	10	AND1
10	1 <u>10</u> 0 (12)	12	JMP1
11	1 <u>11</u> 0 (14)	14	INC1

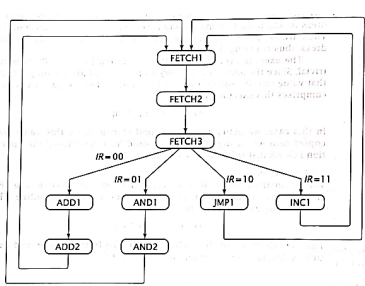- Now, we can assign counter value 9 to ADD2 and 11 to AND2



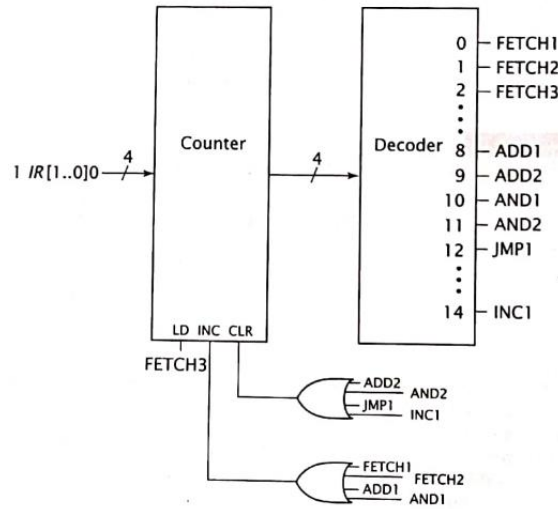- So, a complete hardwired control unit is:



- For Counter, INC, CLR and LD signals are needed.
- INC is asserted when control unit is traversing sequential states, during Fetch1, Fetch2, JMP1 and INC1
- LD is asserted at end of fetch cycle during stateFetch3.
- CLR is asserted at the end of each execute cycle to return to fetch cycle. This happens during ADD2, AND2, JMP1 and INC1

# Some Few Examples:

# Example 1:

Instruction	Instruction Code	Operation
JMP1	00AAAAAA	$PC \leftarrow AAAAAA + 1$
INC2	01XXXXXX	$AC \leftarrow AC + 2$
ADD1	10AAAAAA	$AC \leftarrow AC + M[AAAAAA] + 1$
SKIP	11XXXXXX	$PC \leftarrow PC + 1$

## Datapath

- Fetch 1:  $AR \leftarrow PC$
- Fetch 2:  $DR \leftarrow M$ ,  $PC \leftarrow PC + 1$
- Fetch 3:  $IR \leftarrow DR[7,6]$ ,  $AR \leftarrow DR[5....0]$
- JMP11:  $PC \leftarrow AR$
- JMP12:  $PC \leftarrow PC + 1$
- INC21:  $AC \leftarrow AC + 1$
- INC22:  $AC \leftarrow AC + 1$
- ADD11:  $DR \leftarrow M$ ,  $AC \leftarrow AC + 1$
- ADD12:  $AC \leftarrow AC + DR$
- SKIP1:  $PC \leftarrow PC + 1$

 


Figure: State diagram



- Students are required to design:
  - Datapath
  - ALU

# Hardwired Control Unit

## Datapath

- **Fetch 1:**  $AR \leftarrow PC$
- **Fetch 2:**  $DR \leftarrow M, \quad PC \leftarrow PC + 1$
- **Fetch 3:**  $IR \leftarrow DR[7,6], \quad AR \leftarrow DR[5....0]$
- **JMP11:**  $PC \leftarrow AR$
- **JMP12:**  $PC \leftarrow PC + 1$
- **INC21:**  $AC \leftarrow AC + 1$
- **INC22:**  $AC \leftarrow AC + 1$
- **ADD11:**  $DR \leftarrow M, \quad AC \leftarrow AC + 1$
- **ADD12:**  $AC \leftarrow AC + DR$
- **SKIP1:**  $PC \leftarrow PC + 1$

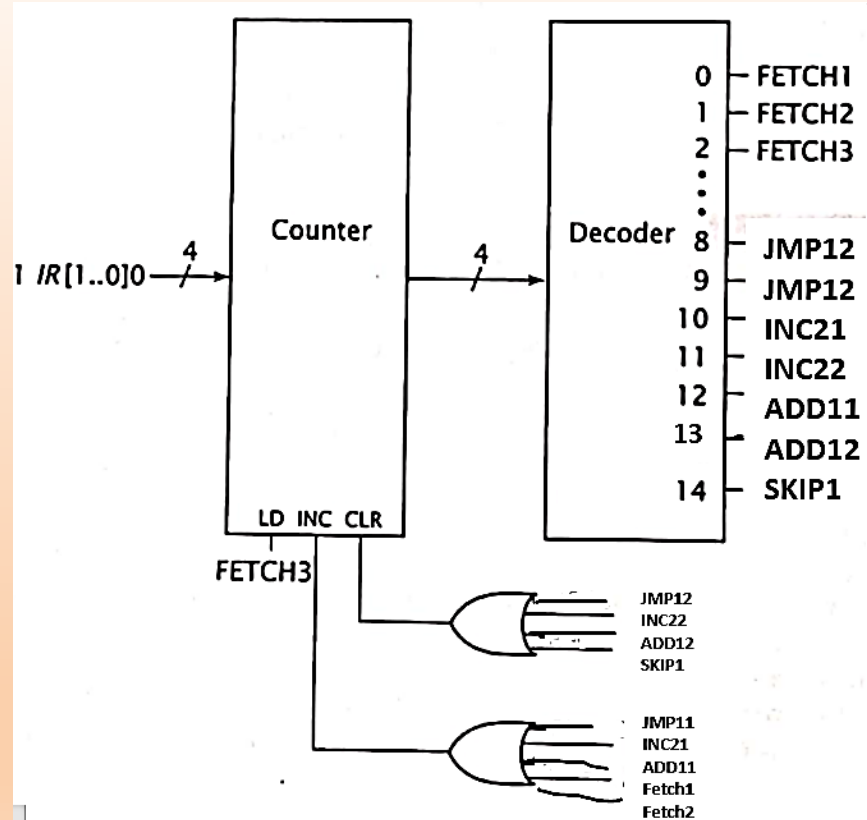


Fig: Hardwired Control Unit for Simple CPU

## Design a CPU that meets the following specifications.


- It can access 64 words of memory, each word being 8 bits wide. The CPU does this by outputting a 6-bit address on its output pins A[5..0] and reading in the 8-bit value from memory on its inputs D[7..0].
- The CPU contains a 6-bit address register (AR) and program counter (PC); an 8-bit accumulator (AC) and data register (DR); and a 2-bit instruction register (IR).
- The CPU must realize the following instruction set.

Instruction	Instruction Code	Operation
COM	00XXXXXX	$AC \leftarrow AC'$
JREL	01AAAAAA	$PC \leftarrow PC + 00AAAAAA$
OR	10AAAAAA	$AC \leftarrow AC \vee M[00AAAAAA]$
SUB1	11AAAAAA	$AC \leftarrow AC - M[00AAAAAA] - 1$


# Solution:
 
## State diagram and RTL code:


- FETCH1:  $AR \leftarrow PC$
- FETCH2:  $DR \leftarrow M, PC \leftarrow PC + 1$
- FETCH3:  $IR \leftarrow DR[7..6], AR \leftarrow DR[5..0]$
- COM1:  $AC \leftarrow AC'$
- JREL1:  $DR \leftarrow M$
- JREL2:  $PC \leftarrow PC + DR[5..0]$
- OR1:  $DR \leftarrow M$
- OR2:  $AC \leftarrow AC \cup DR$
- SUB11:  $DR \leftarrow M$
- SUB12:  $AC \leftarrow AC + DR'$



# ALU:

 

# Control unit:

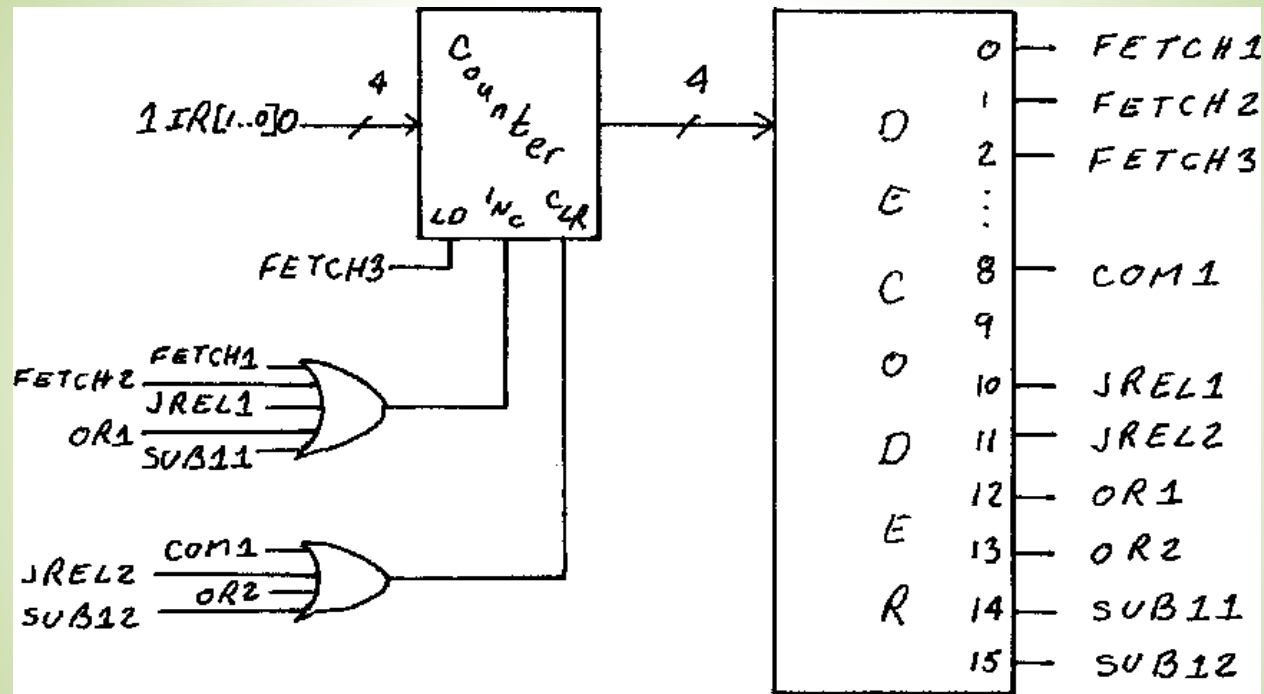

# Assignment:

- Design a CPU that has 6-bit address register (AR), 6-bit program counter (PC), 8-bit data register (DR) and 2-bit instruction register (IR). The CPU must execute the following instructions:

Instruction	Instruction code	Operation
COM	00xxxxxx	$AC \leftarrow \overline{AC}$
AND	01AAAAAA	$AC \leftarrow AC \wedge M[AAAAAA]$
JREL	10AAAAAA	$PC \leftarrow PC + AAAAAA$
SKIP	11xxxxxx	$PC \leftarrow PC + 1$

- Show the RTL code for fetch and execute cycles for each instruction and draw state diagram.
- Show the final register section
- Show the ALU Design
- Show hardwired control unit for same CPU.

# Solution:

- Show the RTL code for fetch and execute cycles for each instruction and
- Draw state diagram.
- Show the final register section and
- Design the ALU
- Show hardwired control unit for same CPU.

- **RTL code:**

Fetch1 :  $AR \leftarrow PC$   
Fetch2 :  $DR \leftarrow M, PC \leftarrow PC+1$   
Fetch3 :  $IR \leftarrow DR[7-6], AR \leftarrow DR[5...0]$   
COM1 :  $AC \leftarrow AC'$   
AND1 :  $DR \leftarrow M$   
AND2 :  $AC \leftarrow AC \wedge DR$   
JREL1 :  $AR \leftarrow DR[5..0]$   
JREL2 :  $PC \leftarrow PC+AR$   
SKIP1 :  $PC \leftarrow PC+1$



# Exam Questions:

1. a) **There is a Very Simple CPU for the given set of Instructions: [PU 2017 Fall]**
- LDA (Load Accumulator with a value from memory) with opcode 00;
  - AND (performing and operation to the content of accumulator with the value at some memory address) with opcode 01;
  - SKIP (skipping an instruction) with opcode 10;
  - DEC (decrementing the value at accumulator) with opcode 11;

Let the instruction width be 8 bits and address is 6 bits. Design the CPU's Register section, state diagram and ALU.

- b) **Design the hardwired control unit for the CPU described in above question. [PU 2017 Fall]**

2. a) There is a very simple CPU for the given set of Instruction: [PU 2017 Spring]

Instruction	Instruction Code	Micro-operation
ADD	00 AAAAAA	$AC \leftarrow AC + M[AAAAAA]$
SUB	01 AAAAAA	$AC \leftarrow AC - M[AAAAAA]$
SKIP	10 XXXXXX	$PC \leftarrow PC + 1$
DEC2	11 XXXXXX	$AC \leftarrow AC - 2$

Let the instruction width be 8 bits and address is 6 bits. Design the CPU's register section, state diagram and ALU.

- b) Design the hardwired control unit for the CPU described in above question. [PU 2017 Spring]

3. a) There is a very simple CPU for the given set of Instruction:  
[PU 2018 Fall]

Instruction	Instruction Code	Operations
STA	00 AAAAAA	$M[AAAAAA] \leftarrow AC$
XNOR	01 AAAAAA	$AC \leftarrow AC \oplus M[AAAAAA]$
JMP	10 AAAAAA	GOTO AAAAAA
SKIP	11 XXXXXX	$PC \leftarrow PC + 1$

Let the instruction width be 8 bits and address is 6 bits. Design the CPU's register section, state diagram and ALU.

- b) Design the hardwired control unit for the CPU described in above question. [PU 2018 Fall]

4. a) There is a very simple CPU for the given set of Instruction:  
[PU 2018 Spring]

Instruction	Instruction Code	Operations
STR	00 AAAAAA	$AC \rightarrow M[AAAAAA]$
NAND	01 AAAAAA	$AC \leftarrow (AC \wedge M[AAAAAA])'$
JMP	10 AAAAAA	$PC \leftarrow AAAAAA$
INC2	11 XXXXXX	$AC \leftarrow AC + 2$

Let the instruction width be 8 bits and address is 6 bits. Design the CPU's register section, state diagram and ALU.

b) Design the hardwired control unit for the CPU described in above question. [PU 2018 Spring]

5. a) There is a very simple CPU for the given set of Instruction: [PU 2019 Spring]

Very simple CPU for the given set of instructions:

Instruction	Instruction Code	Operations
STR	00 AAAAAA	$AC \rightarrow M[AAAAAA]$
AND	01 AAAAAA	$AC \leftarrow AC \wedge M[AAAAAA]$
JMPR	10 AAAAAA	$PC \leftarrow PC + AAAAAA$
DEC2	11 XXXXXX	$AC \leftarrow AC - 2$

Let the instruction width be 8 bits and address is 6 bits. Design the CPU's register section, state diagram and ALU.

- b) Design the hardwired control unit for the CPU described in above question. [PU 2019 Spring]

6. For a very simple CPU, has the following instruction set. Show the state diagram, register section, ALU design.  
[PU 2020 Spring]

Operation	Instruction Code	Instruction
$M[AAAAAA] \leftarrow AC$	00AAAAAA	STA
$AC \leftarrow M[AAAAAA]$	01AAAAAA	LDA
$AC \leftarrow AC + 2$	10XXXXXX	INC
$AC \leftarrow AC'$	11 XXXXXX	COM

# End of chapter 4