

Chapter 2

Computer Organization


Er. Shiva Ram Dam
Assistant Professor
Pokhara University

Contents:

1. Basic Computer Organization
2. System Buses
3. Instruction Cycles
4. CPU organization
5. Memory sub-system, organization and interfacing
6. IO sub-system organization and interfacing

 
1. Basic Computer Organization

- This organization has three main components:
 - CPU,
 - memory subsystem, and
 - IO subsystem




Structural view of Computer System

| | |
|-------------------------------|----------------------------------------------------------------------------------------------------------------|
| CPU | Controls the operation of the computer and performs its data processing functions; also referred as processor. |
| Main Memory | Stores data |
| I/O | Moves data between the memory and its external environment |
| System Interconnection | Some mechanism that provides for communication among CPU, main memory and I/O. it is done through system bus. |

 


Structural view of Computer System (Contd.)

| | |
|-----------------------------|---------------------------------------------------------------------------------|
| Control Unit: | Controls the operation of the CPU and hence the computer. |
| ALU: | Performs the computer's data processing function. |
| Registers: | Provides storage internal to the CPU. |
| CPU interconnection: | Some mechanisms that provide for communication among the CU, ALU and registers. |

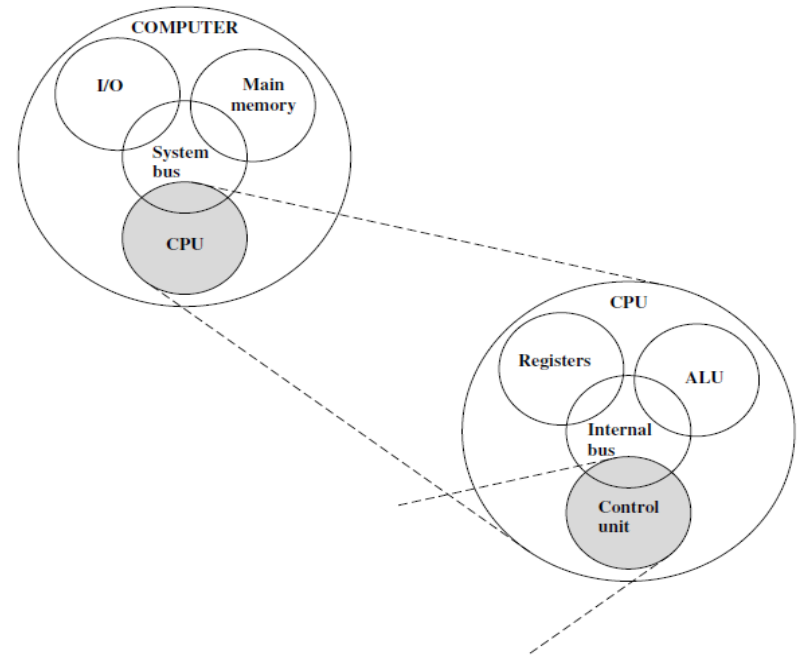

Structural view of Computer System (Contd.)

| | |
|-----------------------------------|-----------------------------------------------------------------------------|
| Control Memory: | The registers which store data related to control operation. |
| Sequential Logic: | Digital circuit whose output depends on current input and state of circuit. |
| CU register & decoder: | Performs storage and interpretation of the instruction. |

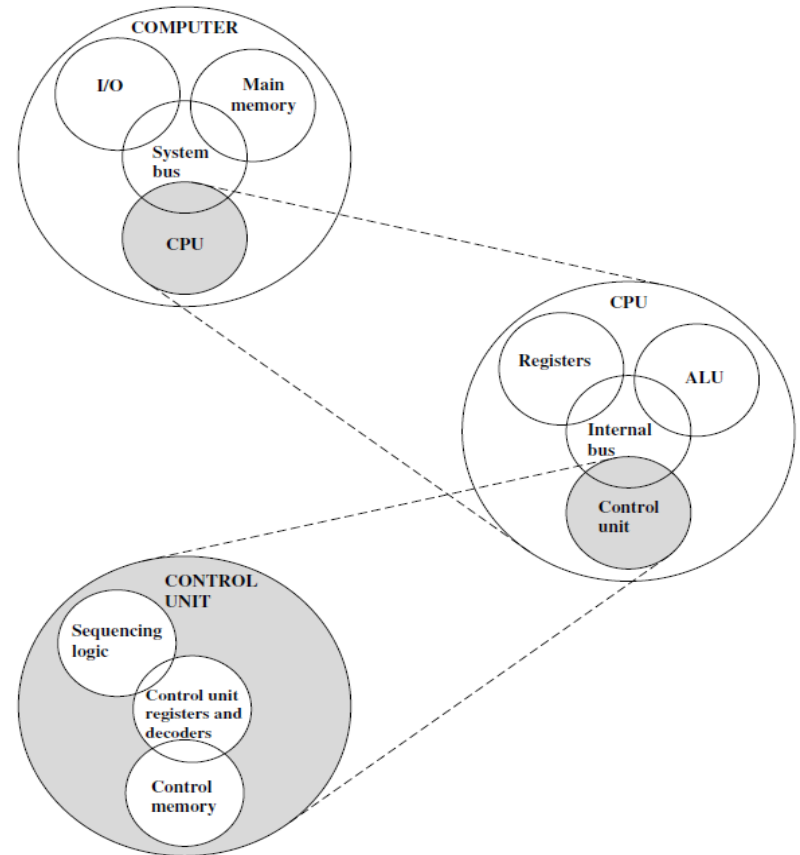

2. System Buses


- Physically, a bus is a set of wires.
- The components of the computer are connected to the buses.
- To send information from one component to another, the source component outputs data onto the bus.
- The destination component then inputs this data from the bus.
- As the complexity of a computer system increases, it becomes more efficient at using buses rather than direct connections between every pair of devices.
- Buses use less space on a circuit board and require less power than a large number of direct connections.
- They also require fewer pins on the chip or chips that comprise the CPU.

2. System Buses (Contd.)


- It is a shared transmission medium. Multiple devices connect to the bus, and a signal transmitted by one device is available for reception by all other devices attached to the bus.
- If two devices transmit during the same time period, their signals will overlap and become garbled.
- Thus, only one device, at a time, can successfully transmit.
- Typically, a bus consists of multiple communication pathways or lines.
- Each line is capable of transmitting signals representing binary 1 or 0.
- An 8-bit unit of data can be transmitted over eight bus lines.
- A bus that connects major computer components (processor, memory, IO) is called a system bus.

2. System Buses (Contd.)


| | |
|----------------------|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| Data Lines | The data lines provide a path for moving data among system modules. These lines, collectively, are called the data bus. |
| Address Lines | The address lines are used to designate the source or destination of the data on the data bus. |
| Control Lines | <p>The control lines are used to control the access to and the use of the data and address lines.</p> <p>Control signals transmit both command and timing information among system modules.</p> <p>Timing signals indicate the validity of data and address information. Command signals specify operation to be performed.</p> |

 

3. Instruction Cycle

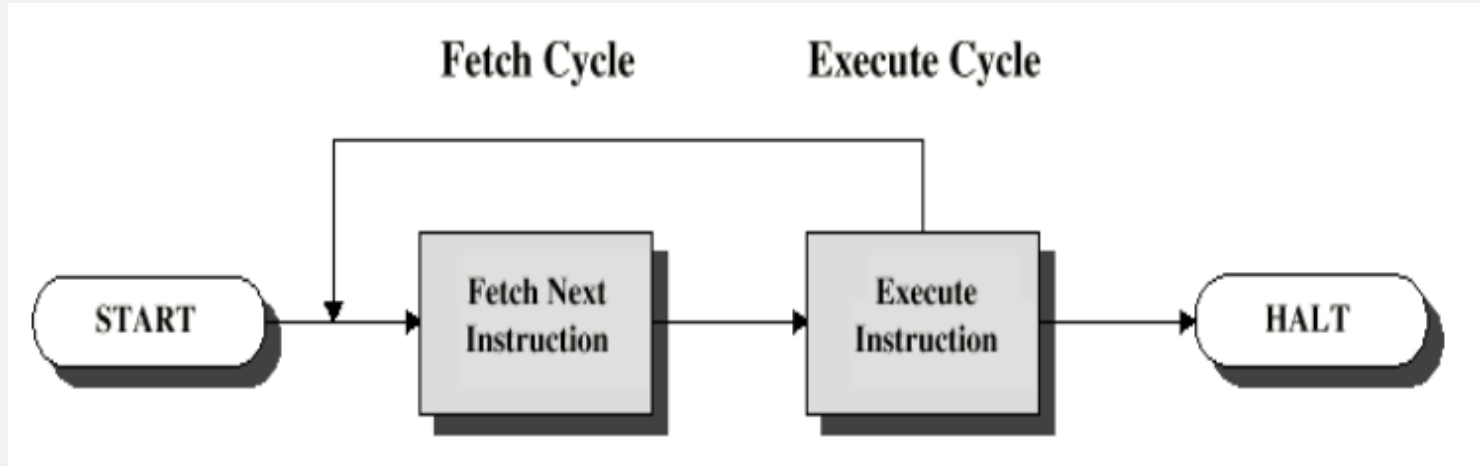


3. Instruction Cycle (Contd.)

 

- The instruction cycle is the procedure a microprocessor goes through to process an instruction.
- First the microprocessor **fetches** or reads, the instruction from memory.
- Then it **decodes** the instruction, determining which instruction it has fetched.
- Finally, it performs the operations necessary to **execute** the instruction.
- Each of these functions- fetch, decode and execute- consists of a sequence of one or more operations.

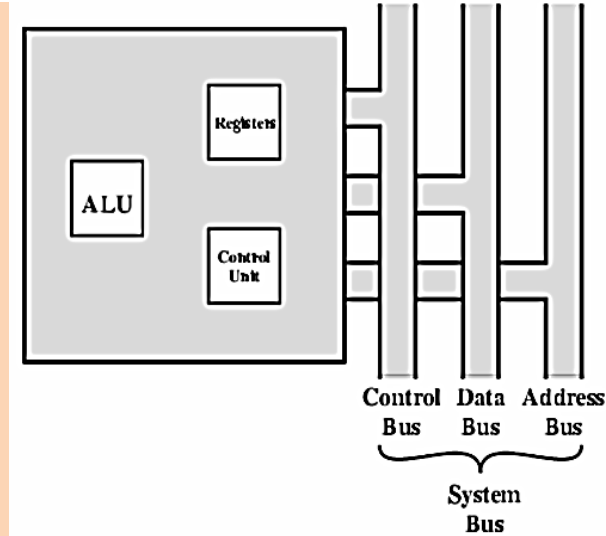4. CPU organization

- CPU consists of three components:
 - ALU,
 - CU and
 - Registers.
- ALU performs arithmetic and logical operation,
- CU provides control signals, and
- registers store binary information and provide very fast information to ALU and out of CPU.
- These components are connected with each other and with external environment through system bus as shown below:



2.4 Memory Sub-system Organization and Interfacing

- Memory is the group of circuits used to store data.
- Two types of Memory:
 1. RAM
 - a) SRAM:
 - More like registers, no need of refresh
 - b) DRAM:
 - Leaky capacitor, needs refresh
 2. ROM
 - a) PROM
 - b) EPROM
 - c) EEPROM
 - d) Flash Memory

RAM

Vs

ROM


- Volatile in nature.
 - Used for reading and writing data in any order as required.
 - Data is stored and read many times to and from this type of memory.
 - Memory cells can be accessed for information transfer from any desired random location.
- Read only memory (ROM) contains a permanent pattern of data that cannot be changed.
 - A ROM is non-volatile, i.e., no power source is required to maintain the bit values in memory.
 - While it is possible to read a ROM, it is not possible to write new data into it.
 - The data or program is permanently presented in main memory and never be loaded from a secondary storage device with the advantage of ROM.

Internal Chip Organization

- Linear organization
- Two-dimensional organization

Linear organization

- Consider an 8 x 2 ROM chip: (Chip is in $2^n \times m$ representation where n is address line and m is data line)
 - Address line = 3
 - Data lines = 2
 - 16 bits of internal storage
 - If $CE = 0$, decoder is disabled and no location is selected. The Tri-state buffer for that location's cell are enabled, allowing data to pass to the output buffers.
 - If $CE = 1$ and $OE = 1$, tri-state buffer for that location cell is enabled and data is output from the chip; otherwise the outputs are tri-stated.

 


Classwork:

- **show the internal linear configuration of a 32x2 memory chip.**


Classwork:

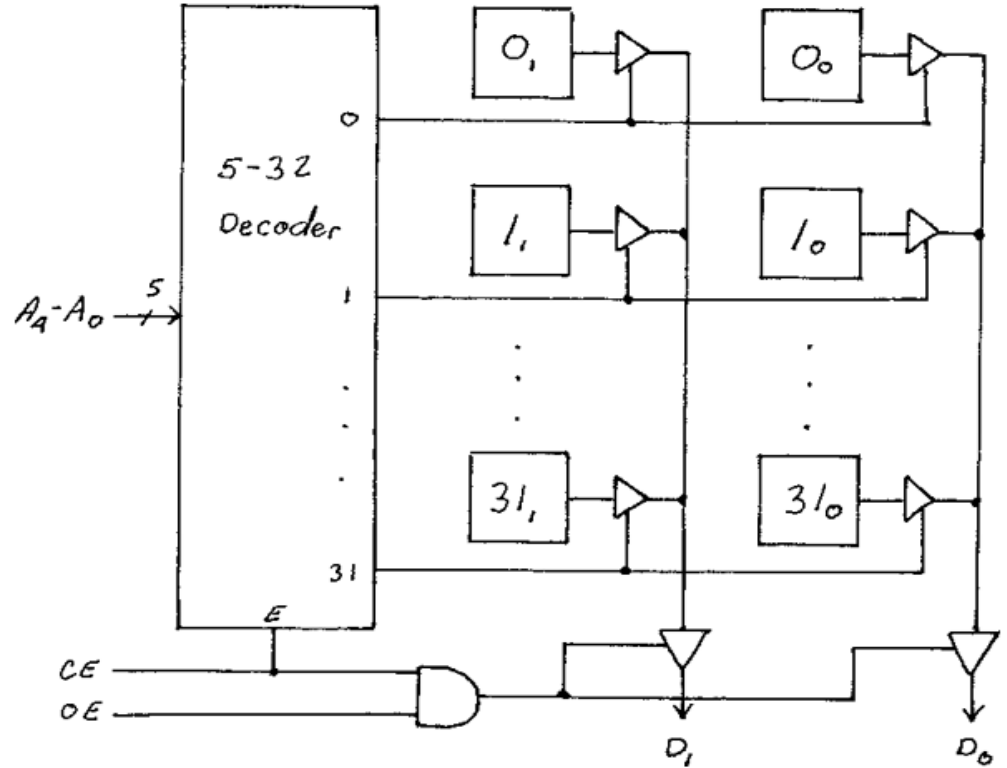- show the internal linear configuration of a 32x2 memory chip.



Two-dimensional organization

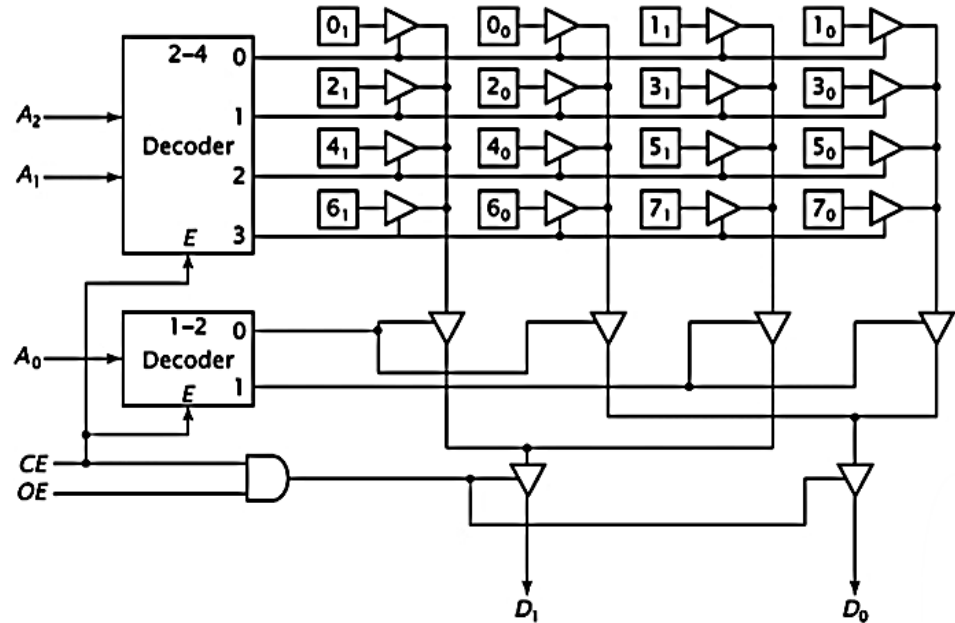- As the number of locations increases, the size of address decoder needed, becomes extremely large.
- To remedy this problem, the memory chip can be designed using multiple dimension of decoding.
- This configuration has four rows with four bits per row; each holds two data values.
- Here,
- $A_0 \rightarrow$ selects one of the 2 locations in a row
- $A_1, A_2 \rightarrow$ selects one of 4 rows.




2.5 Memory Sub system Configuration

- There is technique for joining memory chips to form a memory subsystem.
- Two or more chips can be combined to generate a memory with more bits per location.
- This is done by linking the corresponding address and control signals of the chips and linking their data pins to various bits of the data bus.


Construction of 8 x 4 ROM from two 8 x 2 ROMs:

 - **Two 8 x 2 chips** can be **combined** to generate an **8 x 4 memory** as displayed in the figure.
- **Both chips get the equal three address inputs** from the bus, and the same chip enables and output enables signals.




Construction of 8 x 4 ROM from two 8 x 2 ROMs:

 - The data chips of the first chips are linked to bits 3 and 2 of the data bus (i.e. D_3 and D_2)
- and those of the other chips are linked to bits 1 and 0 (i.e. D_1 and D_0)
- When the CPU reads data, it locates the address on the address bus.
- Both chips read in address bits A_2 , A_1 , and A_0 and implement their internal decoding..



Construction of 8 x 4 ROM from two 8 x 2 ROMs:

- If the **CE** (Chip Enable) and **OE** (Output Enable) signals are **activated**, the **chips output their data onto the four bits** of the data bus.
- Because the address and enable signals are equal for both chips, **either both chips and neither chip is active** at any given time.
- The device never has only one of the two, active.
- For this reason, they facilitate as only a single 8 x 4 chip at least until the CPU is concerned.

 

Construction of 16 x 2 ROM from two 8 x 2 ROM chip:

- Instead of generating wider words, chips can be combined to make more words.
- The similar two 8 x 2 chips could alternatively be configured as a 16 x 2 memory subsystem.


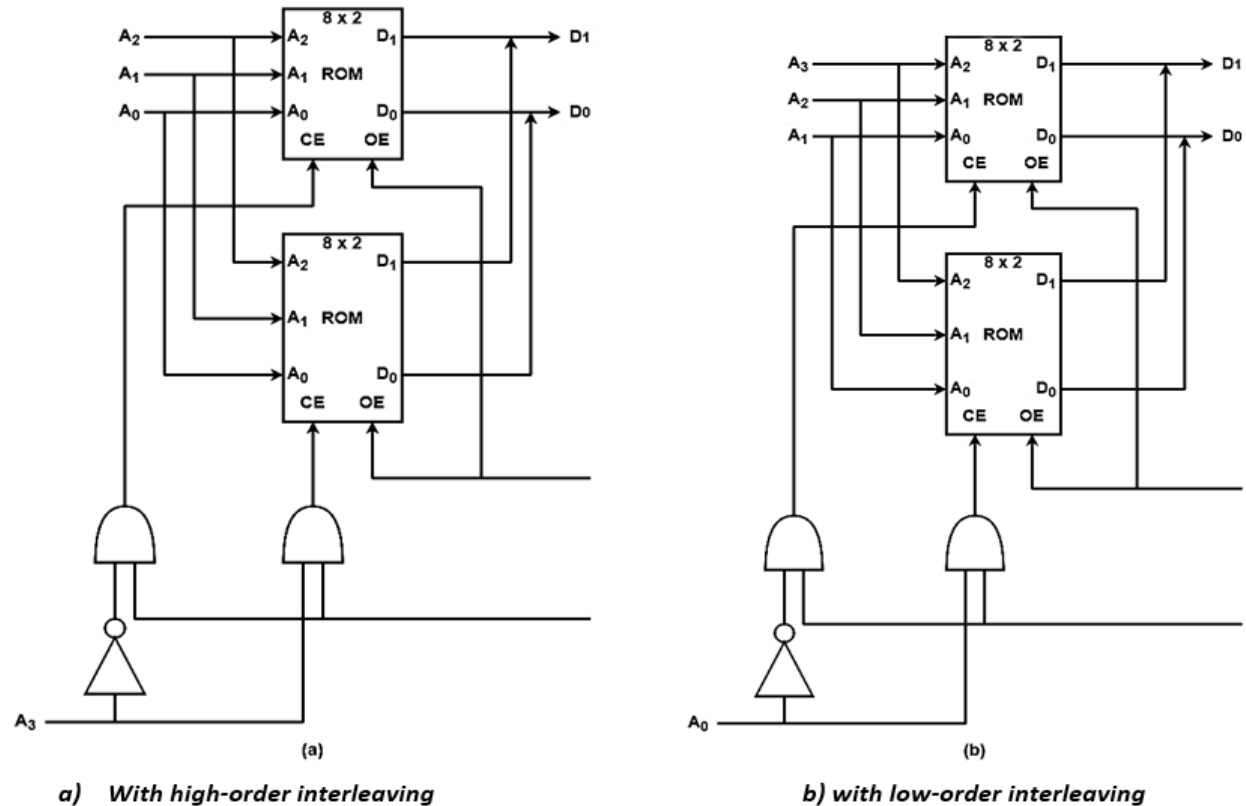


Figure: A 16 x 2 memory subsystem constructed from two 8 x 2 ROM chip


Using high-order interleaving

- The configuration in figure (a) uses **high-order interleaving**. All memory locations inside a chip are contiguous within system memory.
- The **upper chip** is configured as memory **locations 0 to 7** (0000 to 0111) and
- the **lower chip** as **locations 8 to 15** (1000 to 1111).
- The upper chip **always** has $A_3=0$ and the lower chip has $A_3=1$.
- This difference can choose one of the two chips.
- When $A_3=0$, the **upper chip is enabled** and the **lower chip is disabled**.
- The output enables can be linked, because only the chip that is enabled with output data.
- Both chips correspond to similar data bits, both are linked to D_1 and D_0 of the data bus

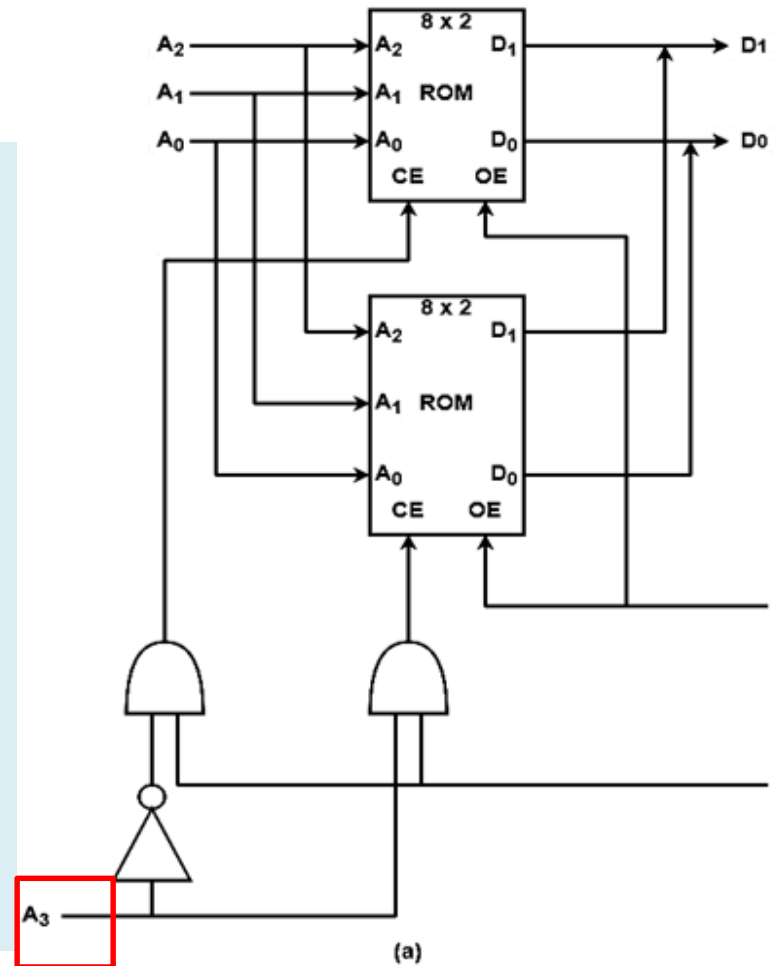

Using low-order interleaving

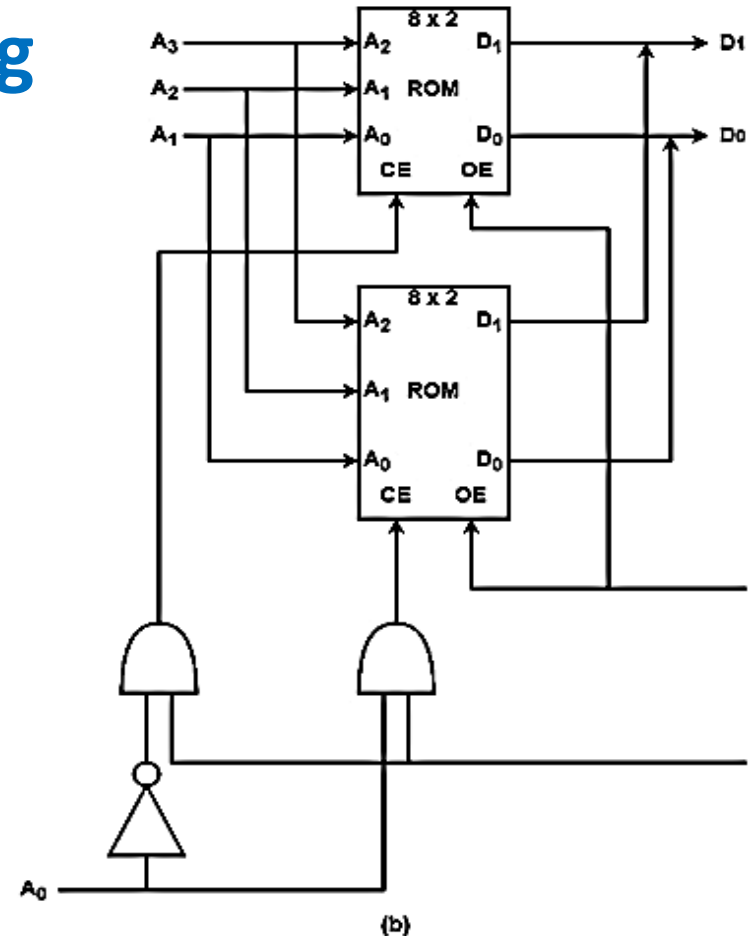- Consider the configuration displayed in figure (b) which uses low-order interleaving.
- The **upper chip is enabled** when $A_0=0$, or by addresses XXX0, in this case, **0, 2, 4, 6, 8, 10, 12, and 14**.
- The **lower chip is enabled** when $A_0=1$, which is correct for addresses **1, 3, 5, 7, 9, 11, 13, and 15**.




Classwork:

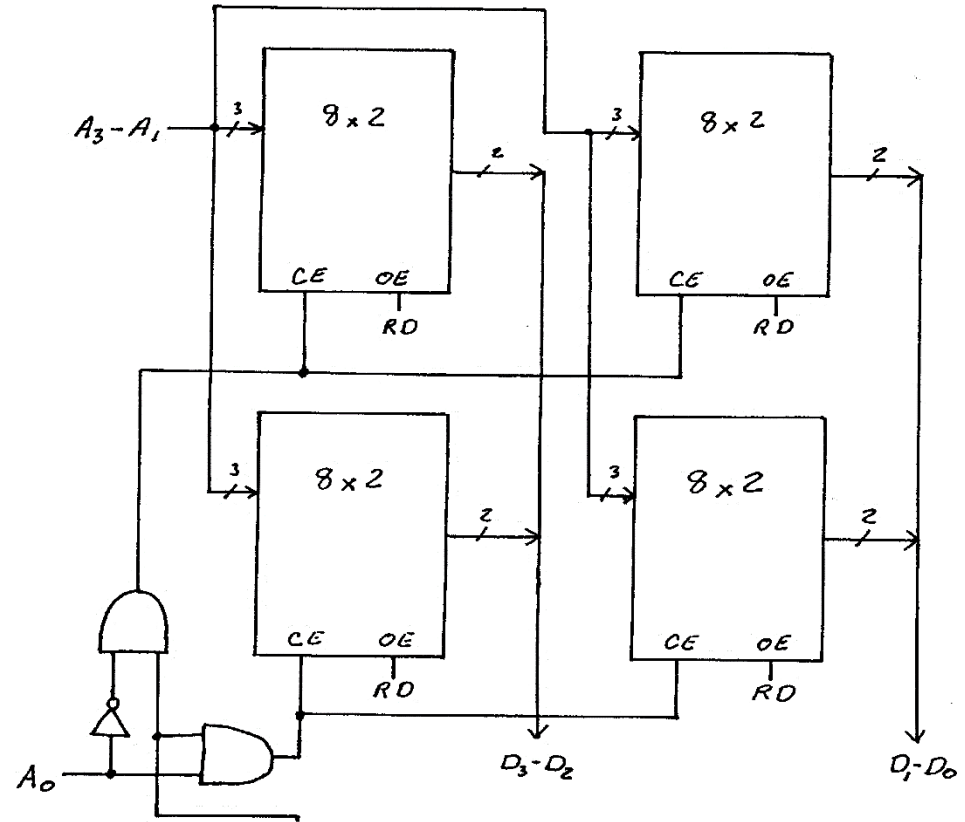1. Design a 16x4 memory subsystem with low order interleaving using 8x2 memory chips for a computer system with an 8-bit address bus.


Classwork:

Design a 16x4 memory subsystem with low order interleaving using 8x2 memory chips for a computer system with an 8-bit address bus.



 
2. Design a 32x 8 memory subsystem with high-order interleaving using 16x2 memory chips for a computer system with an 8-bit address bus.

Design a 32x 8 memory subsystem with high-order interleaving using 16x2 memory chips for a computer system with an 8-bit address bus.




3. Design a 32x8 memory subsystem with low order interleaving using 16x2 memory chips for a computer system with an 8-bit address bus.

 - 2. Design a 32x8 memory subsystem with low order interleaving using 16x2 memory chips for a computer system with an 8-bit address bus.



 6. I/O subsystem Organization and Interfacing

- The I/O subsystem is treated as an independent unit in the computer.
- The CPU initiates I/O command generally as Read, Write, Scan, etc.
- As shown in figure:
 - The **I/O device is connected to the computer system address, data and control buses.**
 - **Each I/O device includes I/O circuitry** that interacts with the buses.



Input device

- The data from the input device goes to the tri-state buffer.
- **When the values on the address bus and control bus are correct, the buffers are enabled and data passes onto the data bus.**
- The CPU, then can read these data.
- The key to this design is the enable logic.
- For the input device, the read signal (RD) should be asserted.
- Figure (b) shows the enable logic for an input device at address 11110000 with 8-bit address and control signals RD and IO/\bar{M} (IO/Memory).

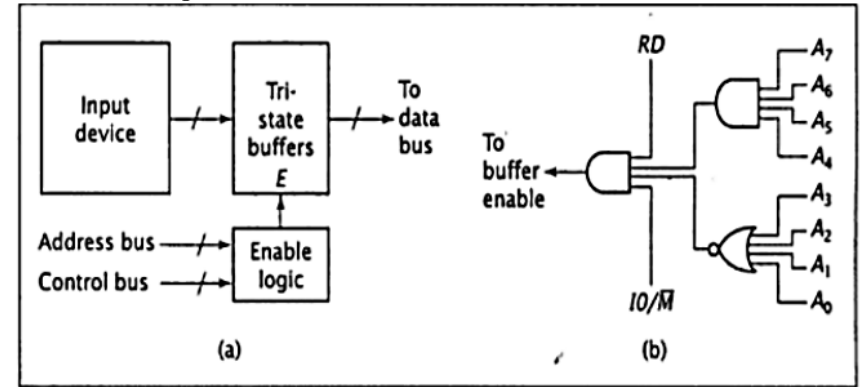


Figure: An Input device: a) with its interface, and b) the enable logic for the tri-state buffers

Output Device:

- For the interface circuit for an output device, the tri-state buffer is replaced by a register.
- **Only the device with the correct address will read it in.**
- The Load logic (LD) plays the role of the enable logic as in the input device.
- **When this logic receives the correct address and control signals, it asserts the LD signal of the register, causing it to read data from the system's data bus.**
- **The output device can then read the data from the register** at its leisure while the CPU performs other tasks.
- The logic to generate the load signal for an output device at address 1111 0000 is shown in figure (b).

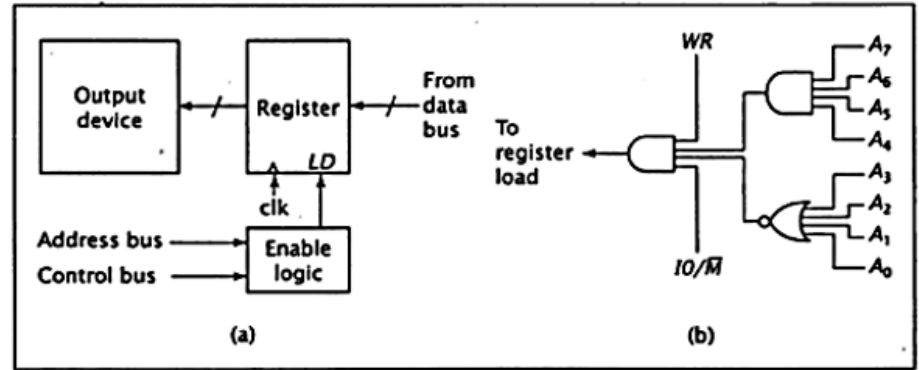


Figure: An Output device: a) with its interface and ,b) the load logic for the register

Bidirectional IO device

- Some devices are used for both input and output. A personal computer's hard disk drive falls into this category.
- Such a device requires a combined interface that is essentially two interfaces, one for input and the other for output.
- Some logic elements, such as the gates that check the address and the address bus, can be used to generate both the buffer enable and register load signals.
- Figure below shows a combined I/O interface for address 1111 0000.



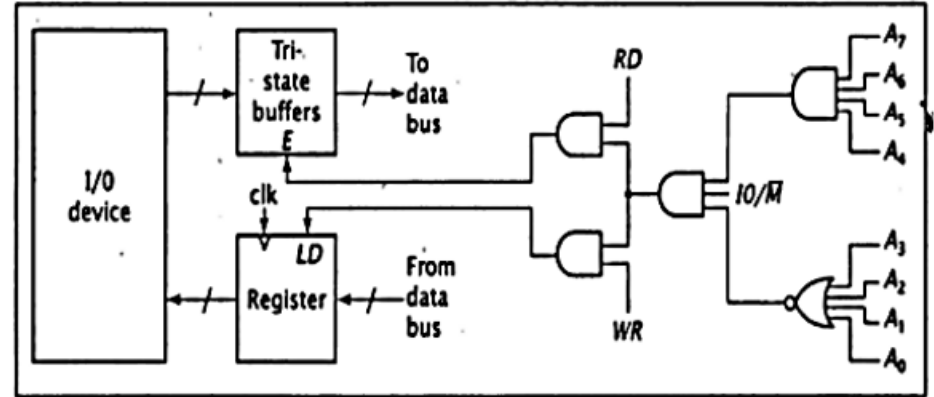
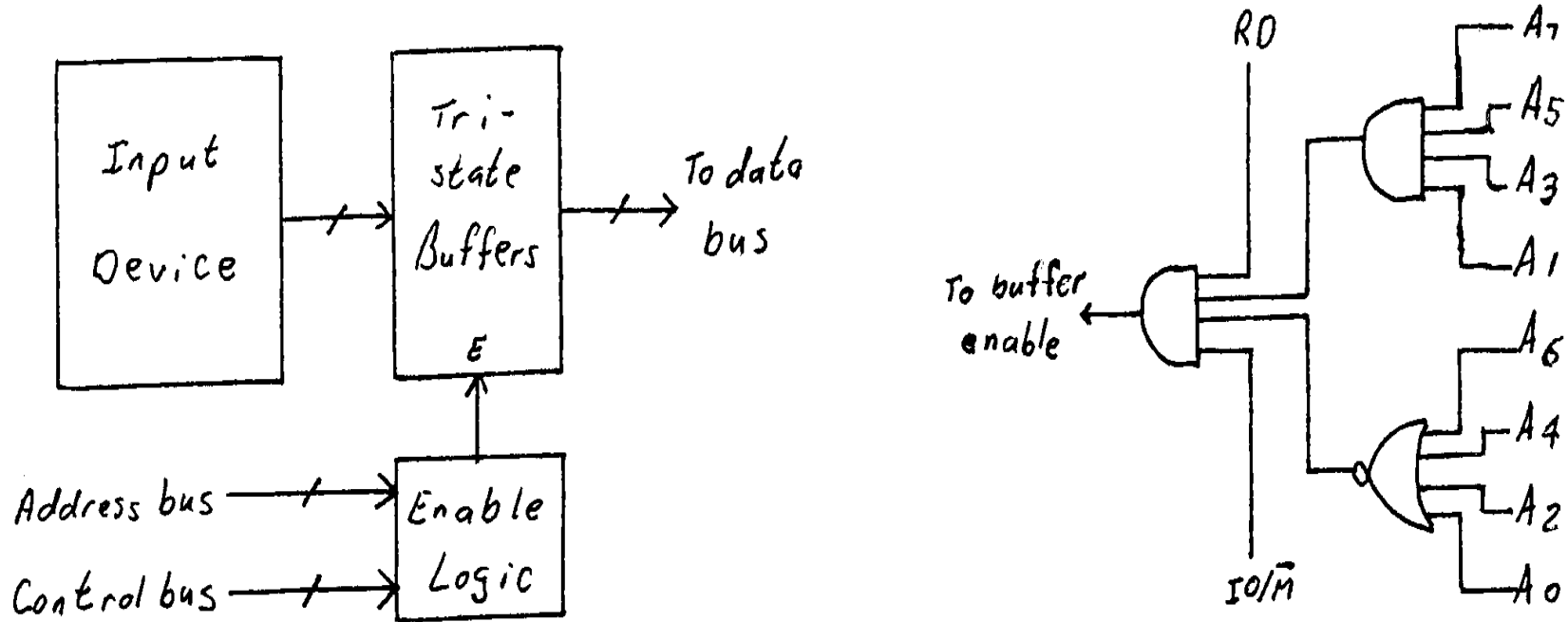


Figure: An bidirectional Input/Output device with its interface and enable/load logic


 
1. Design an interface for an input device which has binary address 1010 1010. Its computer system uses isolated I/O.



 
2. Design an interface for an input device which has binary address 1010 1010. Its computer system uses memory mapped I/O.



 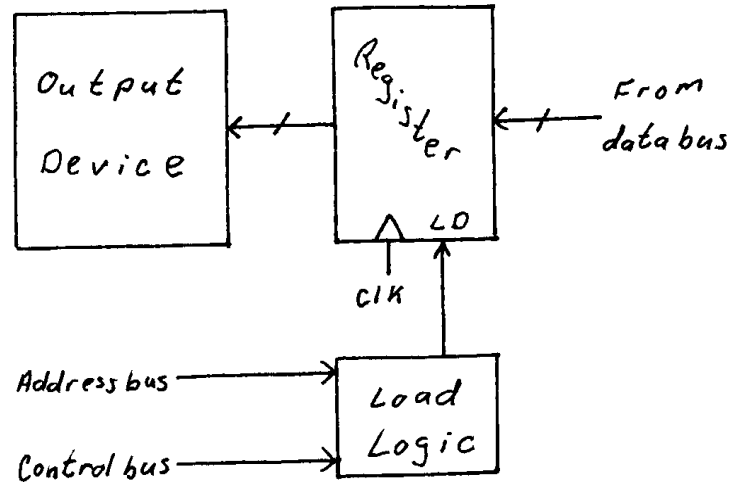
3. Design an interface for an output device which has binary address 0011 1001. Its computer system uses isolate I/O.



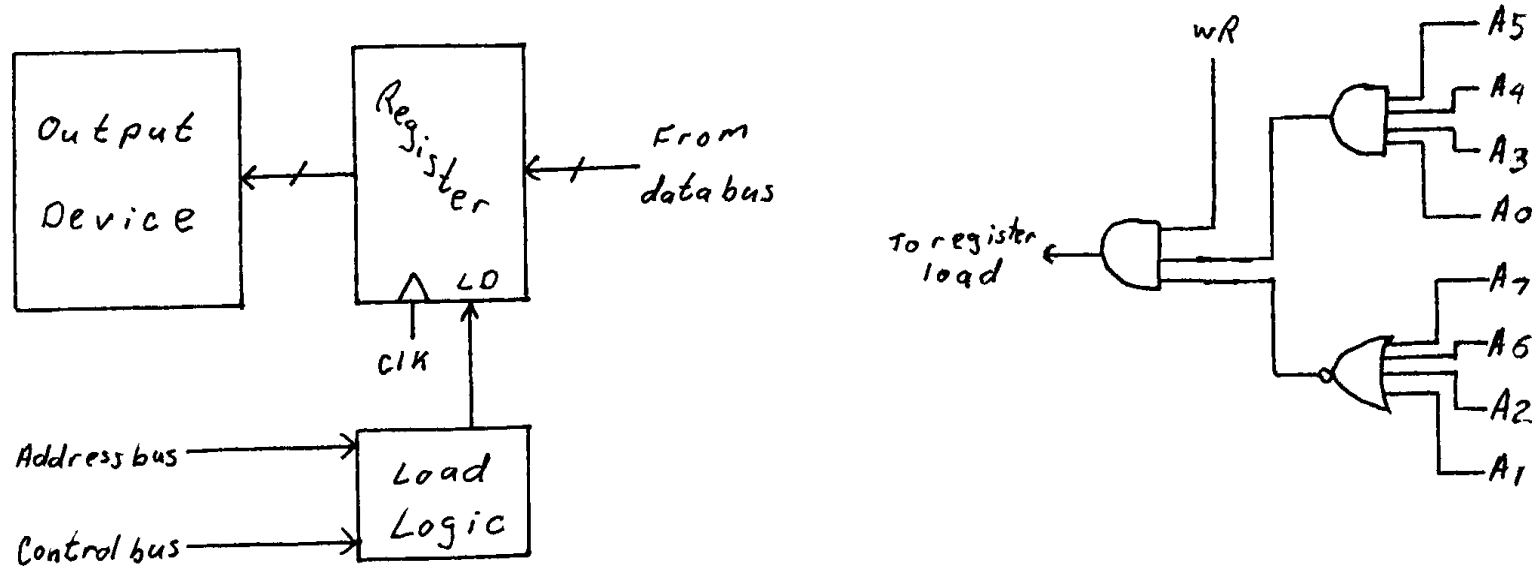4. Design an interface for an output device which has binary address 0011 1001. Its computer system uses memory mapped I/O.



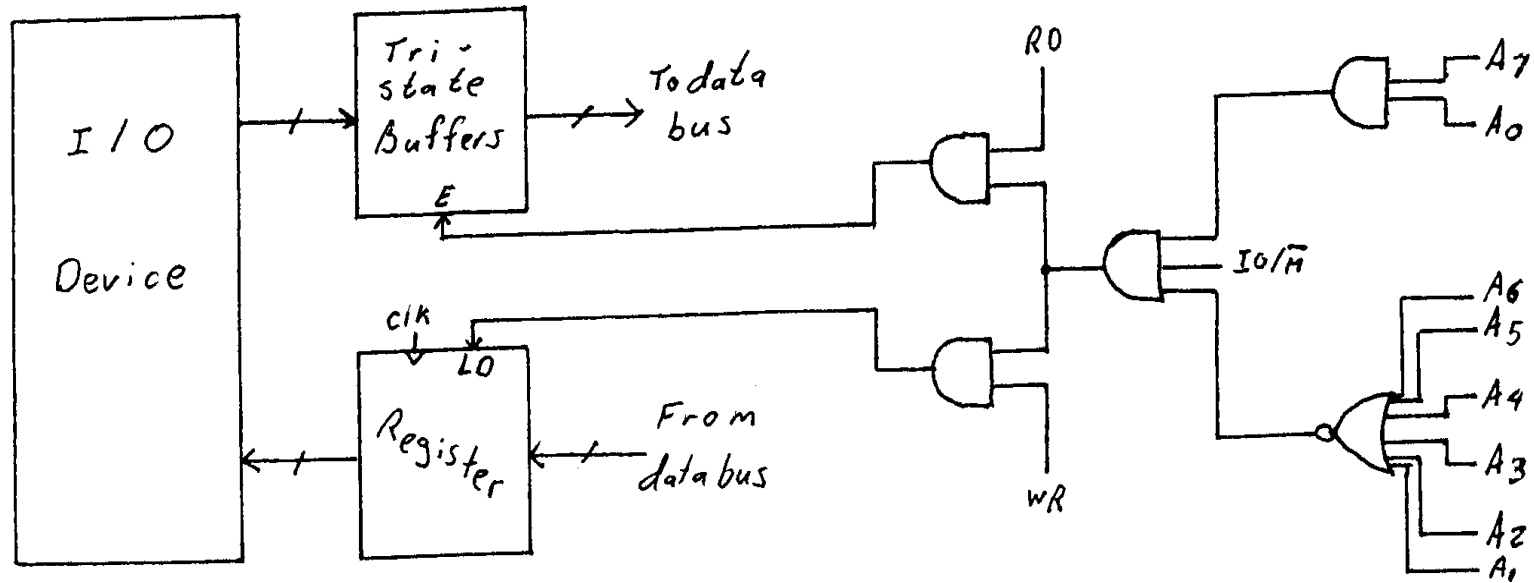5. Design an interface for a bidirectional Input/Output device that has binary address 1000 0001. Its computer system uses Isolated I/O.



A computer system with 8-bit data bus and 8-bit control bus uses isolated I/O. It has 64 bytes of ROM starting at 00H constructed using 64 x 4 chips; 128 bytes of RAM, starting at address 40H constructed using 32 x 8 chips; an input device with READY signal at address 40H; and an output with no READY signal at address 80H. Show the design for this system. Include all enable and load logic.

A computer system with 8-bit data bus and 8-bit control bus uses isolated I/O. It has 64 bytes of ROM starting at 00H constructed using 64×4 chips; 128 bytes of RAM, starting at address 40H constructed using 32×8 chips; an input device with READY signal at address 40H; and an output with no READY signal at address 80H. Show the design for this system. Include all enable and load logic.

Solⁿ: Requirements: 8 bit data and control bus
 64 bytes of ROM constructed by 64×4 chips starting at 00H
 128 bytes of RAM constructed by 32×8 chips starting at 40H
 I/P device with READY signal at address 40H
 O/p device with no READY signal at " 80H


Here, $00H = 0_{10} = 0000\ 0000_2$
 $40H = 64_{10} = 0100\ 0000_2$
 $80H = 128_{10} = 1000\ 0000_2$

For 64 bytes of ROM, last address $\rightarrow 63_{10} \rightarrow 00111111 = 3FH$
 " 128 " " RAM, " " $\rightarrow 64 + 128 - 1 = 191_{10} = BFH$

For 4 RAMs, each will have $128/4 = 32$ bytes:

A computer system with 8-bit data bus and 8-bit control bus uses isolated I/O. It has 64 bytes of ROM starting at 00H constructed using 64 x 4 chips; 128 bytes of RAM, starting at address 40H constructed using 32 x 8 chips; an input device with READY signal at address 40H; and an output with no READY signal at address 80H. Show the design for this system. Include all enable and load logic.

| Memory | A ₇ | A ₆ | A ₅ | A ₄ | A ₃ | A ₂ | A ₁ | A ₀ | Address | Binary value |
|------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|---------|--------------|
| ROM | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 00H | 0 |
| | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 3FH | 63 |
| RAM 1 2 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 40H | 64 |
| | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 5FH | 95 |
| RAM 2 3 | 0 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 60H | 96 |
| | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 7FH | 127 |
| RAM 3 4 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 80H | 128 |
| | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 9FH | 159 |
| RAM 4 5 | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | A0H | 160 |
| | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | BFH | 191 |

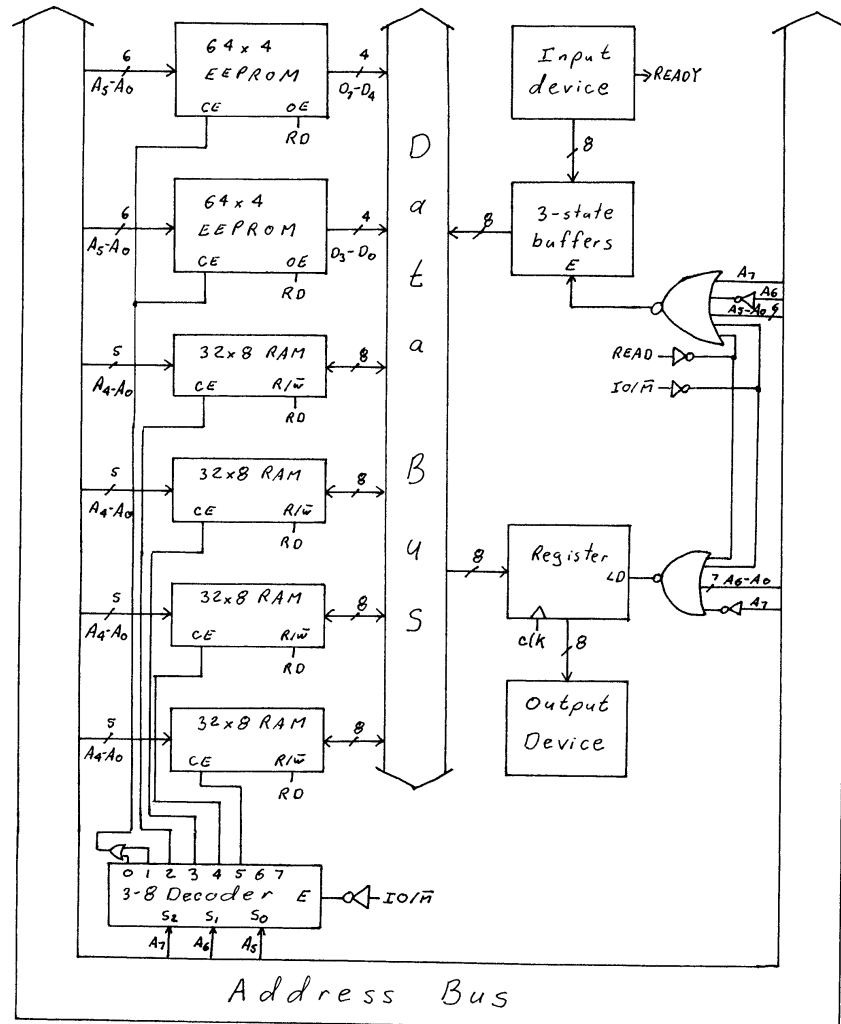

End of chapter